



**RAHEIN EDUCATION**  
www.raheineducation.com

**PHYSICS**

# **RAHEIN EDUCATION PVT. LTD.**

**CONTACT: 9205010851**

**Website: [www.raheineducation.com](http://www.raheineducation.com)**

**BY**

**Asst. Prof. Tarun Kumar Gautam**

**(B.Tech, M.Tech, PhD (P))**

**Currently working in Jamia Hamdard, (HSC), Delhi**

**Working on Nano Technology with Rise University, USA**

**Author of 8 books regarding Physics and Engineering Subject.**

**Ex-Faculty of Rajshree Institute of Management & Technology (RMIT), Braeilly, Uttar Pradesh**

**Ex-Faculty of Assistant professor in Krishna Engineering Collage (KEC), Ghaziabad, Uttar Pradesh**





**Member of Educational Project in University of Petroleum and Energy Studies (UPES), UK**





**RAHEIN EDUCATION**  
www.raheineducation.com

**PHYSICS**

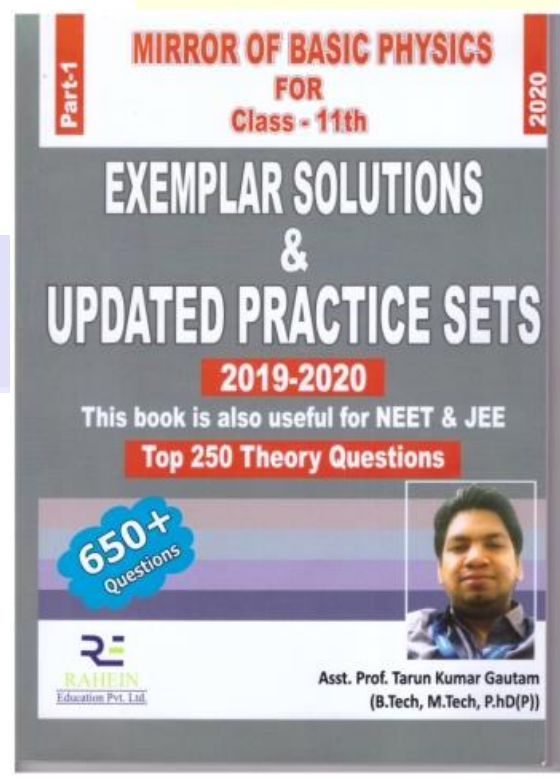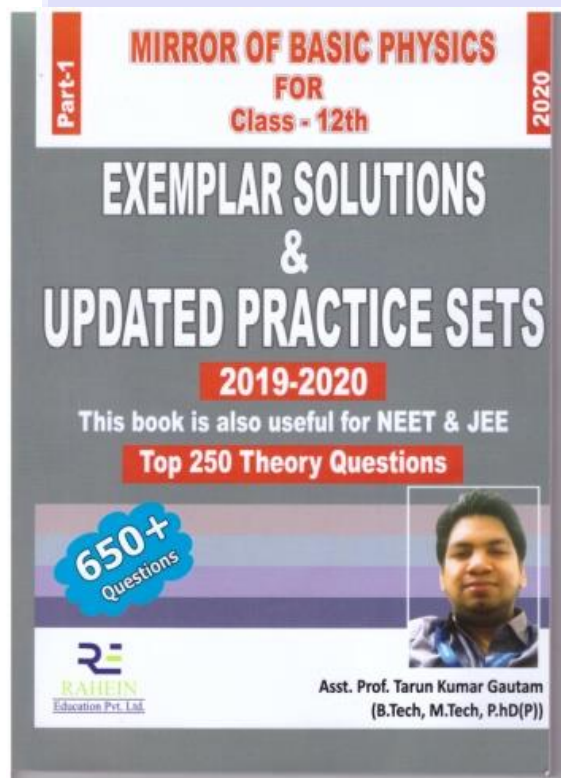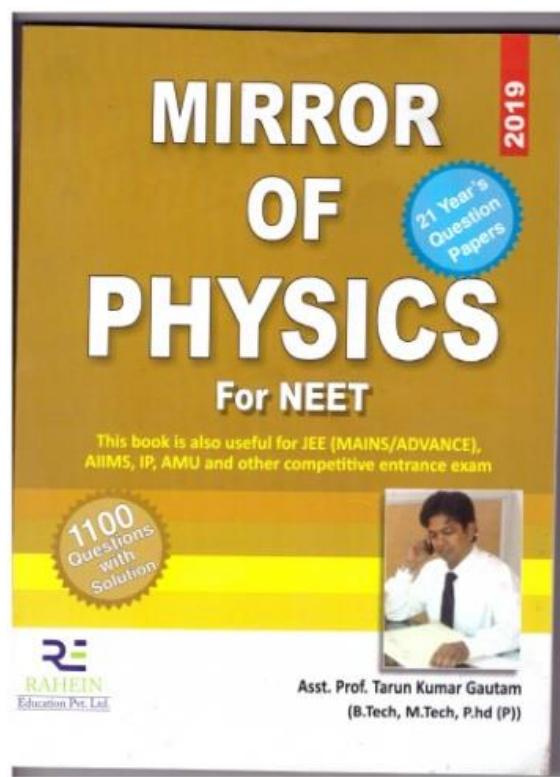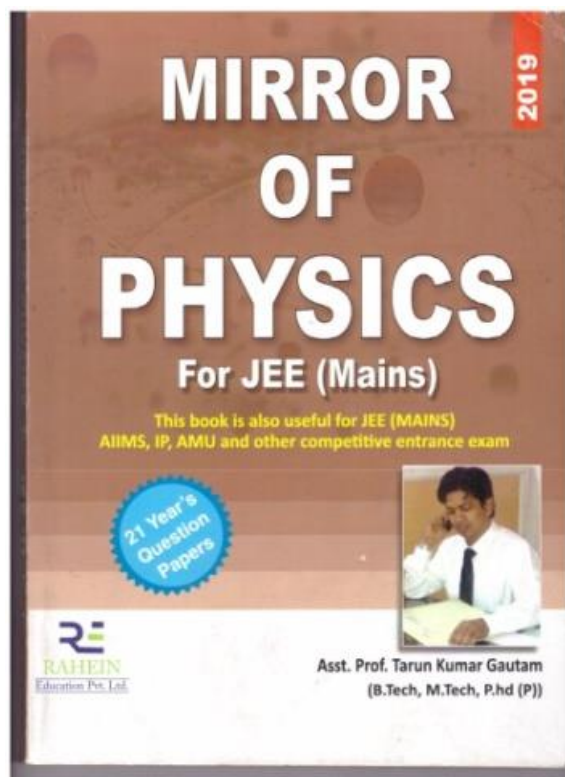


## Chapter-7

### (Alternating Currents)


AC  $\rightarrow$  Alternating Current

DC  $\rightarrow$  Direct Current

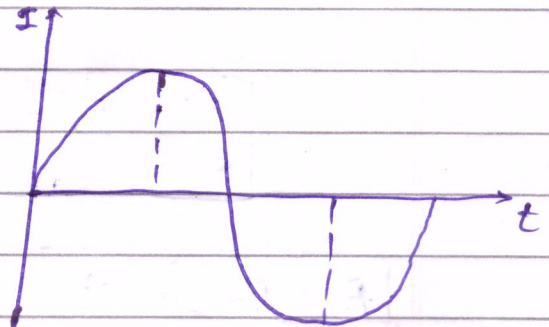Current change with time  
is called "Alternating current."




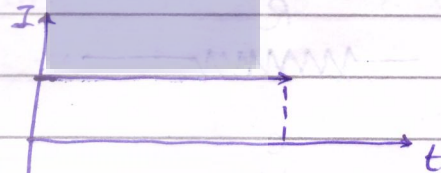Current not change with time  
is called "Direct current"




$$I = I_0 \sin(\omega t)$$

$$I = I_0 \cos(\omega t)$$

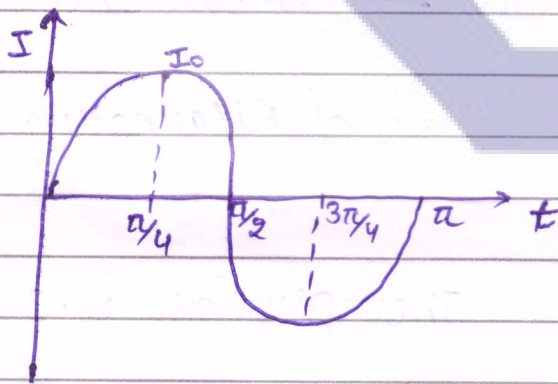

$$I = I_0 \sin \omega t$$

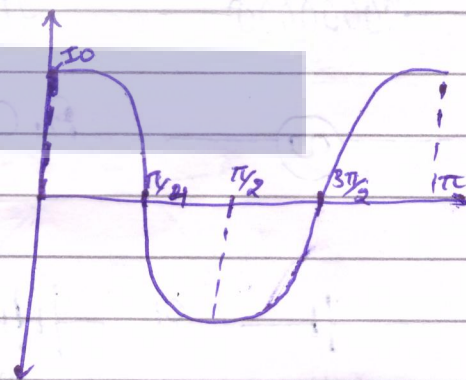

$$I = I_0 \cos \omega t$$

$$\left. \begin{aligned} t &= T/4 \\ t &= T/2 \\ t &= 3T/4 \\ t &= T \end{aligned} \right\}$$

$T \Rightarrow$  Time period

$t \rightarrow$  Instant time



Here,  $\omega = 2\pi\nu$  frequency

$$\omega = 2\pi \frac{1}{T}$$


time period


$$V = E = \text{Potential / emf}$$


$$V = E = IR$$


$$E = E_0 \sin \omega t$$



$$E = E_0 \cos \omega t$$

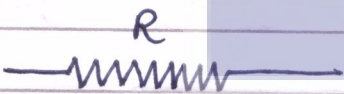
①  Resistor → Resistance

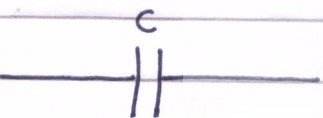②  Capacitor → Capacitance

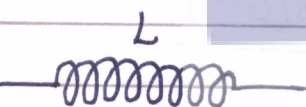③  Inductor → Inductance

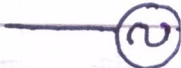④  A.C (sign of Alternating Current)

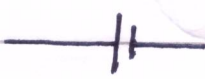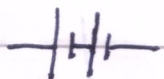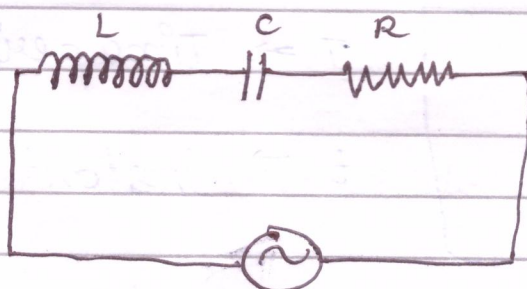
⑤  or  They provide D.C Current  
Cell Battery



LCR circuit



## A.C Circuit with Resistance (R)

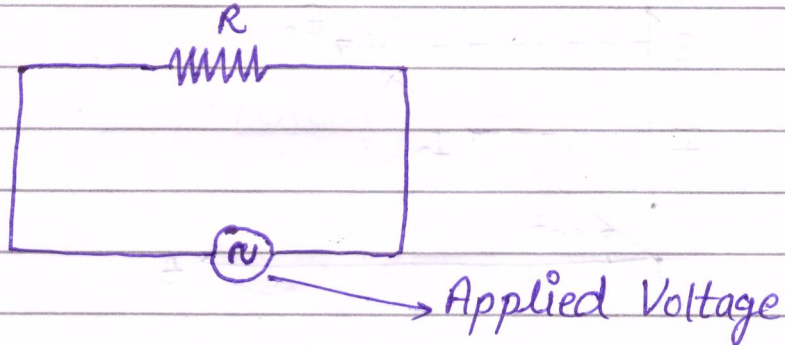

$$E = E_0 \sin \omega t$$

$$I \times R = E_0 \sin \omega t$$

$$I_0 \rightarrow \text{max current}$$

$$I = \left[ \frac{E_0}{R} \right] \sin \omega t$$

$$E_0 \rightarrow \text{max. voltage}$$

$$I = I_0 \sin \omega t$$


Note

$$\left. \begin{aligned} E &= E_0 \sin \omega t \\ I &= I_0 \sin \omega t \end{aligned} \right\}$$

### graphical / wave diagram


Phase angle  $[\phi = 0]$

Voltage & Current are  
in same phase.

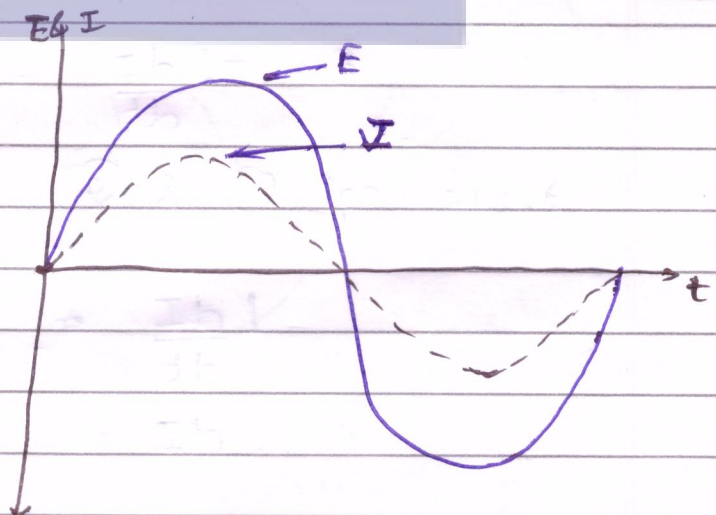


- Amplitude of Current is less than the amp. of the Voltage
- Voltage on currents are in phase current each other in pure current.

## Phasor Diagram

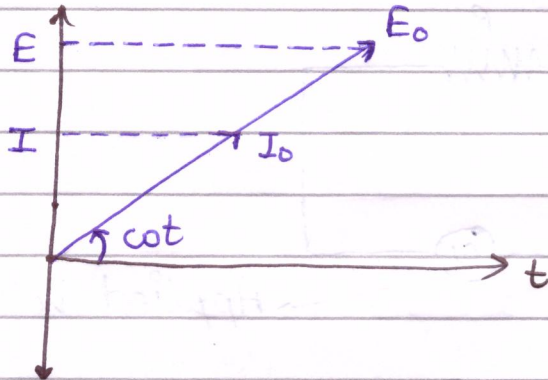
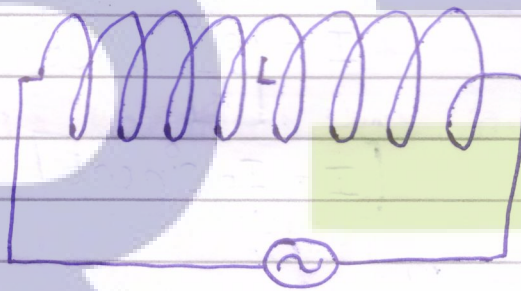
## A.C Circuit containing Inductance only



$$E = E_0 \sin \omega t$$

①

Emf in Inductor

$$E = -L \frac{dI}{dt} \quad \text{--- (2)}$$

From eq<sup>n</sup> ① & ②

$$L \frac{dI}{dt} = E_0 \sin \omega t$$

$$dI = \frac{E_0}{L} \sin \omega t \, dt$$

Integrate both side

$$\int dI = \int \frac{E_0}{L} \sin \omega t \, dt$$



$$\int dI = \frac{E_0}{L} \int \sin \omega t \, dt$$

$$I = \frac{E_0}{L} \left( -\frac{\cos \omega t}{\omega} \right)$$


$$I = -\frac{E_0}{L} \left( \frac{\cos \omega t}{\omega} \right)$$

$$I = -\frac{E_0}{L\omega} \cos \omega t$$

Using the identity,  $-\cos \omega t = \sin \left[ \omega t - \frac{\pi}{2} \right]$

$$I = \left( \frac{E_0}{L\omega} \right) \sin \left[ \omega t - \frac{\pi}{2} \right]$$
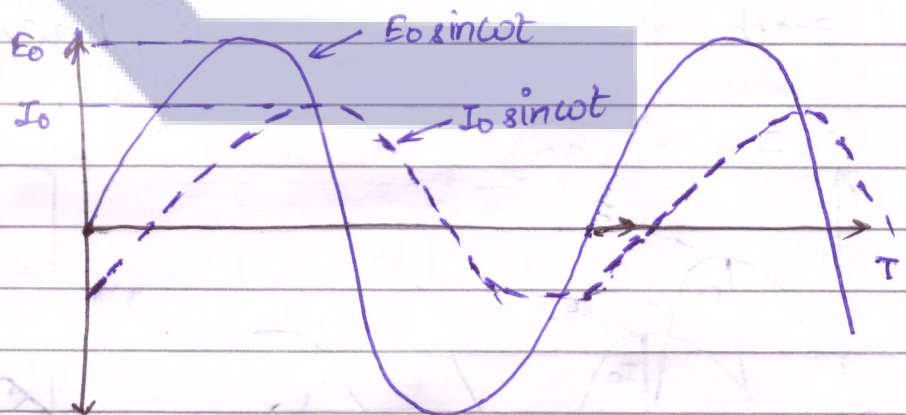
$$I = I_0 \sin \left[ \omega t - \frac{\pi}{2} \right]$$




Inductive Reactance

$$I = \frac{E_0}{L\omega}$$

$$\text{As, } E = IR, \quad I = \frac{E}{R}$$

$X_L$  is Inductive Reactance,  $X_L = \omega L$

$$X_L = 2\pi \nu L$$

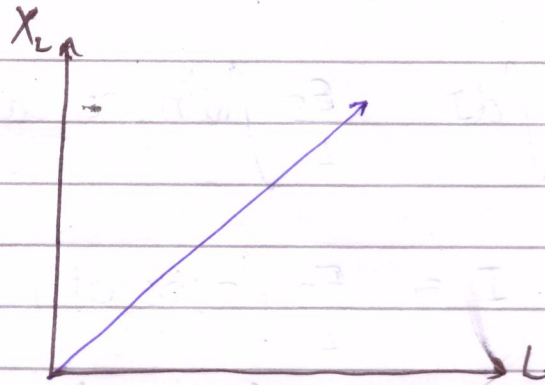

Note


①  $E = E_0 \sin \omega t$

②  $I = I_0 \sin(\omega t - \frac{\pi}{2})$


- Current is lag behind by  $\frac{\pi}{2}$  from voltage.
- Voltage is lead by  $\frac{\pi}{2}$  from current.

Phase difference =  $\frac{\pi}{2}$

graph

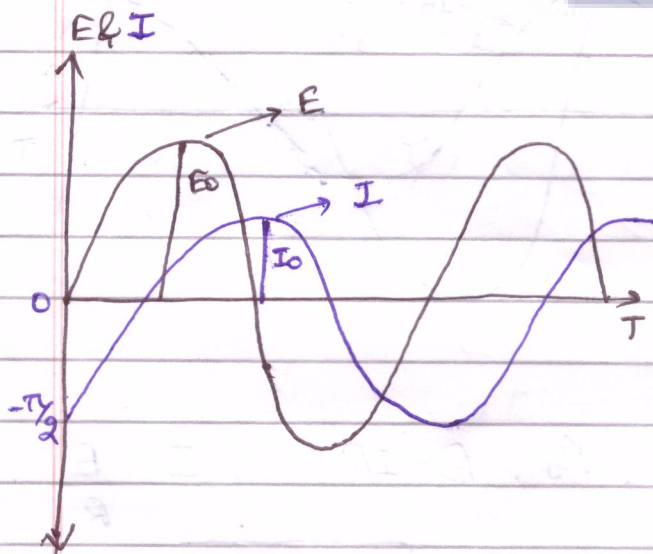

Phase diagram

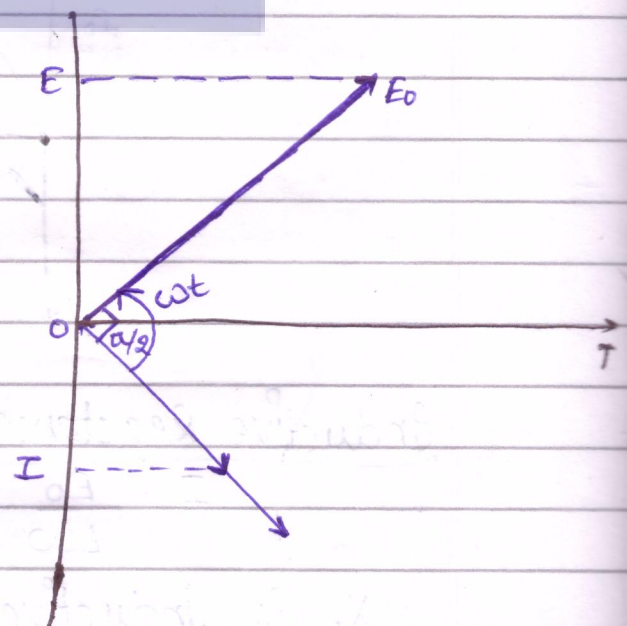

$X_L = \omega L$


Unit = ohm ( $\Omega$ ) = Hsec<sup>-1</sup>



①

$$E = E_0 \sin \omega t$$

Resistance

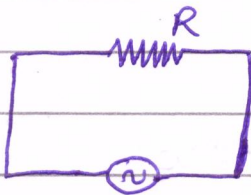


$$E = E_0 \sin \omega t$$

$$I = I_0 \sin \omega t$$

$$\phi = \text{phase angle} = 0$$

Inductor

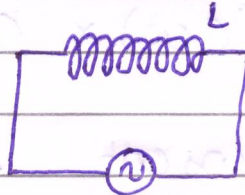

$$E = E_0 \sin(\omega t)$$


$$I = I_0 \sin\left(\omega t - \frac{\pi}{2}\right)$$

$$\text{phase angle, } \phi = -\frac{\pi}{2}$$

$$X_L = \omega L$$

Inductive Reactance

Capacitor

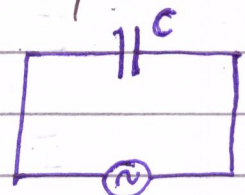

$$E = E_0 \sin(\omega t)$$


$$I = I_0 \sin\left(\omega t - \frac{\pi}{2}\right)$$

$$\text{phase angle} \rightarrow \phi = +\frac{\pi}{2}$$

$$X_C = \frac{1}{\omega C}$$

Capacitive Reactance

A.C Circuit Containing Capacitor only.

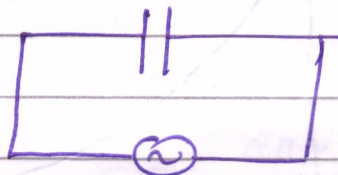

$$\rightarrow Q = CV$$

$$V = \frac{Q}{C}$$

$$Q = CV = CE$$

$$Q = C \times E_0 \sin \omega t$$

Differentiation both side

$$I = \frac{dQ}{dt} = \frac{d}{dt}(CE_0 \sin \omega t)$$

$$I = CE_0 \frac{d(\sin \omega t)}{dt}$$

$$I = CE_0 \cos \omega t \times (\omega)$$

$$I = E_0 (C\omega) \times \cos \omega t$$


$$I = \frac{E_0 \cos \omega t}{1/\omega} \Rightarrow I_0 \cos \omega t$$

$$I = I_0 \cos \omega t \Rightarrow I = I_0 \sin\left(\omega t + \frac{\pi}{2}\right)$$

$$X_C = \frac{1}{\omega C}$$

$$\omega = 2\pi f$$

$$X_C = \frac{1}{2\pi f \times C}$$

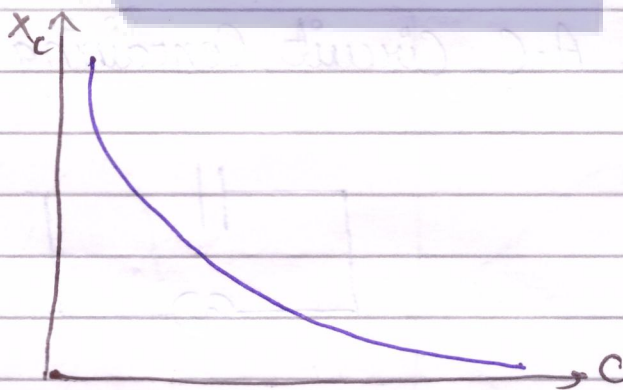

Note  $E = E_0 \sin \omega t$


$$I = I_0 \sin\left(\omega t + \frac{\pi}{2}\right)$$

$$\phi = +\frac{\pi}{2}$$


Current lead by  $\frac{\pi}{2}$  for voltage.  
Voltage lag behind  $\frac{\pi}{2}$  for current.



## Graphical Representation

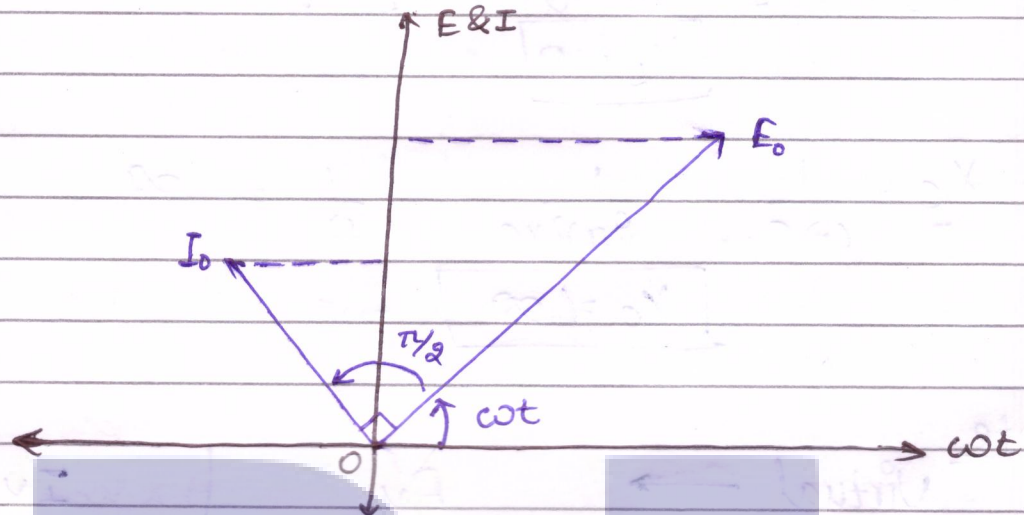

## Phase Diagram

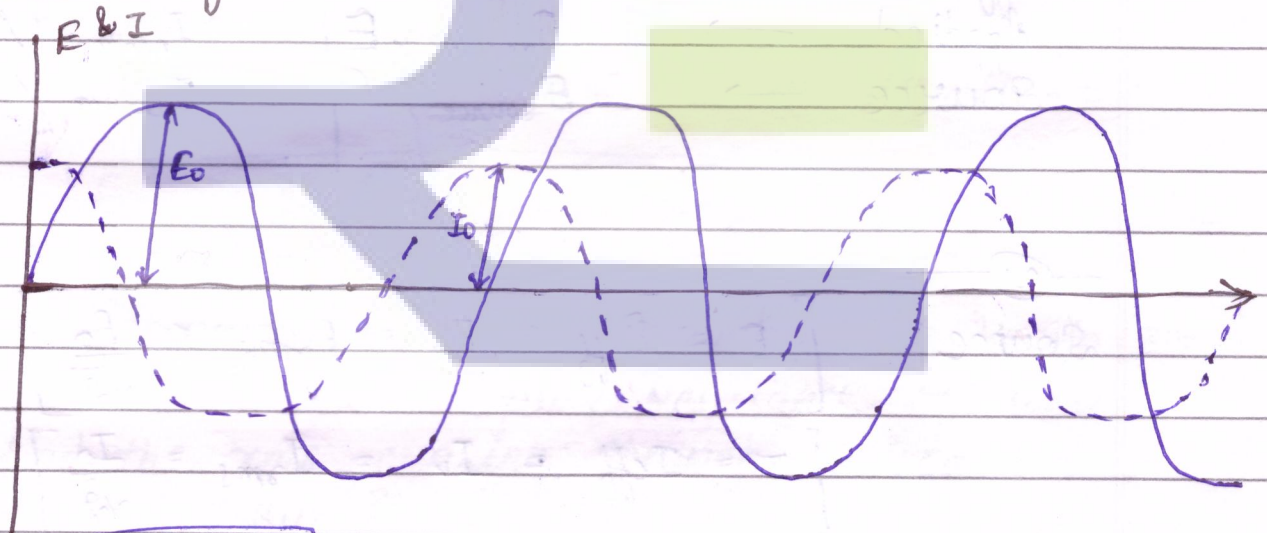

$$X_c = \frac{1}{\omega C}$$

$$X_c = \frac{1}{2\pi \nu \times C}$$

Unit

$$\Omega = \frac{1}{\text{sec}^{-1} \times f} \Rightarrow \boxed{\Omega = \text{sec } f^{-1}}$$

Unit  $\boxed{\Omega = \text{sec } f^{-1}}$

DC circuit  $\rightarrow \omega = 0$

$$X_L = \omega L = 2\pi\omega L = 0$$

$$\boxed{X_L = 0}$$

$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi\omega C} = \frac{1}{0} = \infty$$

$$\boxed{X_C = \infty}$$

Note

Virtual $\rightarrow$	$E_v$	$I_v$
root mean square $\rightarrow$	$E_{rms}$	$I_{rms}$
effective $\rightarrow$	$E_{eff}$	$I_{eff}$
Applied $\rightarrow$	$E_{applied}$	$I_{applied}$
Source $\rightarrow$	$E_{source}$	$I_{source}$

(2)

$$\text{Source} \quad \left[ E = E_{eff} = E_v = E_{rms} = \frac{E_0}{\sqrt{2}} \right]$$

$$\left[ I = I_{eff} = I_v = I_{rms} = \frac{I_0}{\sqrt{2}} \right]$$

Amplitude of source

\*  $E_0 = \text{Max. voltage / Potential emf}$

\*  $I_0 = \text{Max. current / current}$   
Amplitude of current



- Instantaneous voltage  $\rightarrow E = E_0 \sin \omega t$
- Instantaneous current  $\rightarrow I = I_0 \sin \omega t$

Ques What will be the Instantaneous voltage for A.C supply of 220 volt & at 50 hertz?

Ans  $E = 220 \text{ volt}$ ,  $\nu = 50 \text{ Hz}$

$$E = \frac{E_0}{\sqrt{2}}$$

$$E_0 = \sqrt{2} \times E$$

$$E_0 = 220 \times \sqrt{2} = 311 \text{ volt}$$

$$E = E_0 \sin \omega t$$

$$E = 311 \sin (2\pi \nu \times t) = 311 \sin (2\pi \times 50 \times t)$$

$$\boxed{E = 311 \sin (100\pi t) \text{ volt}}$$

Ques An alternating voltage given by,  $V = 140 \sin (3.14t)$  connected across a pure Resistance of  $50 \Omega$ , find the rms current through Resistance?

Ans  $V = 140 \sin (3.14t)$

$$\omega, 3.14 \Rightarrow 2\pi \nu = 3.14$$

$$V = V_0 \sin (3.14t)$$

$$\nu = \frac{3.14}{2\pi}$$

$$E_0 = I_0 \times R, \quad E = 140$$

$$E_0 = IR \rightarrow I_0 = \frac{E_0}{R} = \frac{140}{50} \Rightarrow \left| I = \frac{I_0}{\sqrt{2}} = \frac{14}{\sqrt{2} \times 5} \right|$$



Ques The Instantaneous Current from A.C source is  $I = 10 \sin(314t)$  what is frequency of source & r.m.s value of current.

Ans

$$I = I_0 \sin(\omega t)$$

$$I = 10 \sin(314t)$$

$$\omega = 314$$

$$\omega = \frac{2\pi \times \text{frequency}}{2\pi} \text{ Hz}$$

$$2\pi \times \text{frequency} = 314$$

$$I_0 = 10$$

$$I_r = \frac{I_0}{\sqrt{2}}$$

$$I_r = \frac{10}{\sqrt{2}}$$

$$I_r = 7.07$$

Ques  $I_1 = 2A$ ,  $I_2 = 3A$ ,  $I_3 = 4A$ ,  $I_4 = 5A$  find the root mean square value of current?

Ans

$$I = \sqrt{\frac{I_1^2 + I_2^2 + I_3^2 + I_4^2}{4}} \Rightarrow \sqrt{\frac{54}{4}} A$$

Ques A light Bulb is rated at 100 watt for 220 volt supply find (a) Resistance of Bulb? (b) Peak voltage of Source? (c) r.m.s current through the Bulb?

Ans

$$P = \frac{V^2}{R} = VI = I^2 R$$

$$\because V = IR$$

$$I = \frac{V}{R}$$



$$(a) R = \frac{V^2}{P} = \frac{220 \times (2)^2}{100} = 484 \Omega$$

$$(b) E_v = \frac{E_0}{\sqrt{2}} \Rightarrow E_0 = E_v \times \sqrt{2} \Rightarrow 220\sqrt{2}$$

$$(c) P = EI \Rightarrow I = \frac{P}{E} = \frac{100}{220}$$

$$P = \frac{V^2}{R} \Rightarrow I^2 R \Rightarrow VI \Rightarrow \frac{\omega}{t}$$

Note

• Resistance:  $\begin{matrix} \longrightarrow V \\ I \end{matrix}$

$$\begin{matrix} E = E_0 \sin \omega t \\ I = I_0 \sin \omega t \end{matrix}$$


• Inductance:  $\begin{matrix} \longrightarrow V \\ I \end{matrix}$

$$\begin{matrix} E = E_0 \sin(\omega t) \\ I = I_0 \sin\left(\omega t - \frac{\pi}{2}\right) \end{matrix}$$

• Capacitor:  $\begin{matrix} \longrightarrow V \\ I \end{matrix}$

$$\begin{matrix} E = E_0 \sin \\ I = I_0 \sin\left(\omega t + \frac{\pi}{2}\right) \end{matrix}$$

AC Circuit containing LCR:

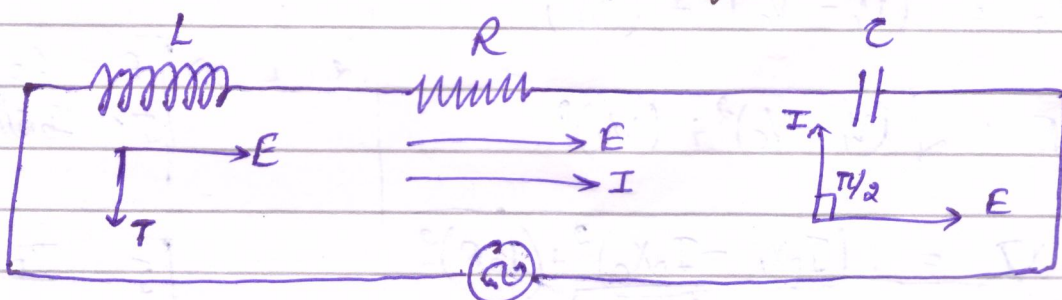





$$I = I_0 \sin \omega t$$
$$E = E_0 \sin \left( \omega t - \frac{\pi}{2} \right)$$


$$\tan \phi = \frac{I_o X_L - I_o X_C}{I_o X_R}$$

$$\tan \phi = \frac{X_L - X_C}{R}$$





## Resistance (R)


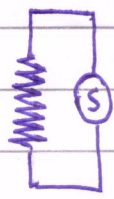


$$E = E_0 \sin(\omega t)$$

$$I = I_0 \sin(\omega t)$$


$$\phi = \text{phase angle} = 0$$

- Current & Voltage are in same phase

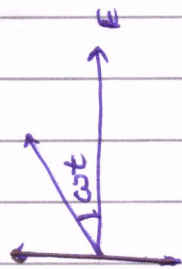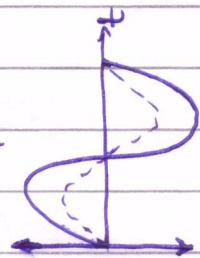

$$V_R = IR$$

## Inductance (L)

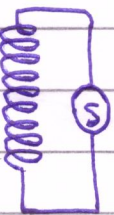


$$E = E_0 \sin(\omega t)$$


$$I = I_0 \sin(\omega t - \frac{\pi}{2})$$

$$\phi = -\frac{\pi}{2}$$

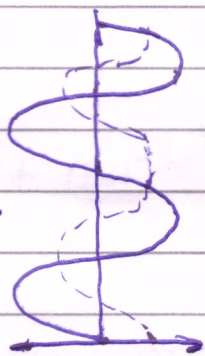
- Current is lag behind by  $\frac{\pi}{2}$  voltage is lead by  $\frac{\pi}{2}$



$$V_L = IX_L, X_L = \omega L$$

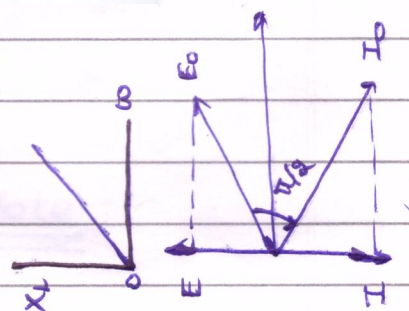

## Capacitor (C)

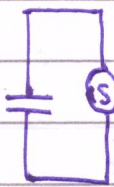


$$E = E_0 \sin(\omega t)$$


$$I = I_0 \sin(\omega t + \frac{\pi}{2})$$

$$\phi = +\frac{\pi}{2}$$

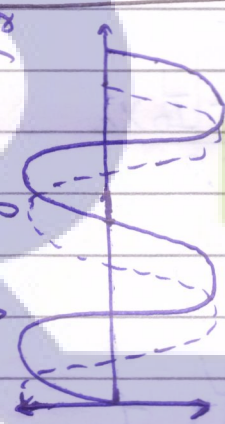
- Current is lead by  $\frac{\pi}{2}$  voltage is lag behind by  $\frac{\pi}{2}$



$$V_C = IX_C, X_C = \frac{1}{\omega C}$$

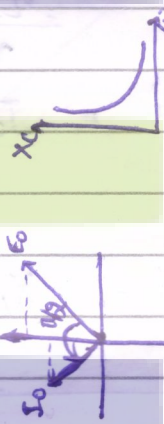

## (LCR)

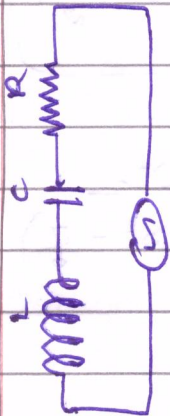

$$E = E_0 \sin(\omega t)$$

$$I = I_0 \sin(\omega t - \phi)$$

$$\tan \phi = \frac{X_L + X_C}{R} = \frac{V_L - V_C}{V_R}$$

$$V_{LCR} = IZ, Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$Z = \text{Impedance}$$

$$V_{LCR} = \sqrt{V_R^2 + (V_L - V_C)^2}$$

Max. volt./emf  
Amplitude of volt./emf  
 $\frac{E_0}{\sqrt{2}}$

$$V_{eff} = E_r = E_{rms} = E_{applied} = E_{source}$$

$$I_{eff} = I_r = I_{rms} = I_{applied} = I_{source}$$

$$\frac{I_0}{\sqrt{2}}$$

Max. current  
Amplitude of current

DATE: \_\_\_\_\_  
PAGE: \_\_\_\_\_



$$P = E_V I_V \cos \phi$$

$$= E_V I_V (1)$$

$$P = E_V I_V$$

$$\text{Power factor} = \cos \phi = \cos(0) = 1$$

$$P = E_V I_V \cos \phi$$

$$= E_V I_V \cos 90 = 0$$

$$P = 0$$

$$\text{Power factor} = \cos(-90) = 0$$

$$P = E_V I_V \cos 90$$

$$= E_V I_V \cos 90 = 0$$

$$P = 0$$

$$\text{Power factor} = \cos(90) = 0$$

Power

$$P = E_V I_V \cos \phi$$

$$\text{① } \cos \phi = \text{Power factor} = \frac{R}{Z}$$

$$\cos \phi = \frac{R}{\sqrt{R^2 + (X_L - X_C)^2}}$$


$$\text{② Quality factor} = \frac{V_L}{V_R} = \frac{V_C}{V_R} = \frac{1}{R} \sqrt{\frac{L}{C}}$$

$$\text{③ Resonance} = X_L = X_C \Rightarrow \omega = \frac{1}{\omega \sqrt{LC}} \Rightarrow \omega = \frac{1}{\sqrt{LC}}$$

Resonance frequency

Note : Impedance Triangle

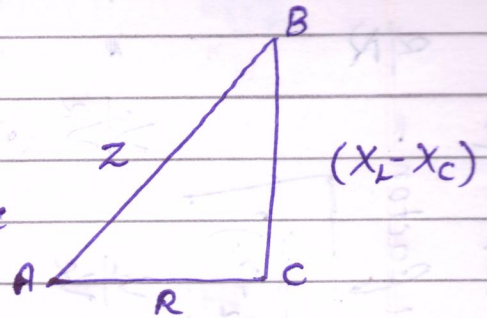
$$(i) \quad Z = \sqrt{R^2 + (X_L - X_C)^2}, \quad \tan \phi = \frac{X_L - X_C}{R}$$



Note :

(i) Resistance (Non-Inductive ckt)

$$X_L = X_C = 0$$

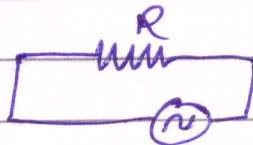

(ii) If  $X_L > X_C \rightarrow$  Inductance Dominating ckt

If  $X_L < X_C \rightarrow$  Capacitance Dominating ckt

Note :

$$Z = \sqrt{R^2 + (X_L - X_C)^2}, \quad P = E_V I_V \cos \phi$$

$$V = \sqrt{V_R^2 + (V_L - V_C)^2}, \quad \cos \phi = \frac{R}{Z}$$

# LR :  $\rightarrow$  C = 0

$$Z = \sqrt{R^2 + X_L^2}, \quad V = \sqrt{V_R^2 + V_L^2}$$

# RC :  $\rightarrow$  L = 0

$$Z = \sqrt{R^2 + X_C^2}, \quad V = \sqrt{V_R^2 + V_C^2}$$

# LC :  $\rightarrow$  R = 0

$$Z = \sqrt{(X_L - X_C)^2}, \quad V = \sqrt{(V_L - V_C)^2}$$



Note:

$$P = \frac{dw}{dt} = EI$$


Energy stored in Capacitor

$$E = \frac{1}{2} CV^2 = \frac{1}{2} QV = \frac{1}{2} \frac{Q^2}{C}$$

Energy Stored in Inductor

Let emf ( $\epsilon$ ) induced in Inductance.

$$E = -L \frac{dI}{dt}$$

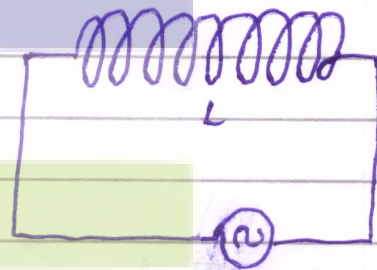

Power:  $P = \frac{dw}{dt} = EI$

Let 'dw' is small work done

$$\frac{dw}{dt} = EI$$

$$dw = EI \cdot dt$$

$$dw = \left( -L \frac{dI}{dt} \right) I \cdot dt$$

$$dw = -L I dI$$

Integration both side

$$\int dw = -L \int I dI$$

$$w = L \left[ \frac{I^2}{2} \right] \Rightarrow w = \frac{1}{2} LI^2$$

Ques 1.5mH Inductor in Circuit stores a maximum energy of 14μJ. What is peak current?

Solu Given,  $L = 1.5\text{mH}$   
 $= 1.5 \times 10^{-3}\text{H}$

$$E = 14\mu\text{J} \Rightarrow 14 \times 10^{-6}\text{J}$$

As we, know,

$$W = \frac{1}{2}LI^2$$

$$14 \times 10^{-6} = \frac{1}{2} \times 1.5 \times 10^{-3} \times I^2$$

$$I^2 = \frac{14 \times 10^{-6} \times 2 \times 10}{1.5 \times 10^{-3}}$$

$$I = \sqrt{\frac{28 \times 10^{-2}}{15}}$$

And we know  $I = \frac{I_0}{\sqrt{2}}$

$$I_0 = I \times \sqrt{2}$$

$$= \sqrt{\frac{28 \times 2 \times 10^{-2}}{15}}$$

Ques 1.5mH Inductor in Circuit stores energy of 14μJ.




## Power Factor ( $\cos \phi$ ) of an A.C

Power Factor is ratio of True power to apperent power.

$$\cos \phi = \frac{\text{True Power}}{\text{Apparent Power}} = \frac{P}{E_v I_v}$$

$$\cos \phi = \frac{R}{Z} = \frac{R \times I}{Z \times I} = \frac{V_R}{V_Z}$$

Ques

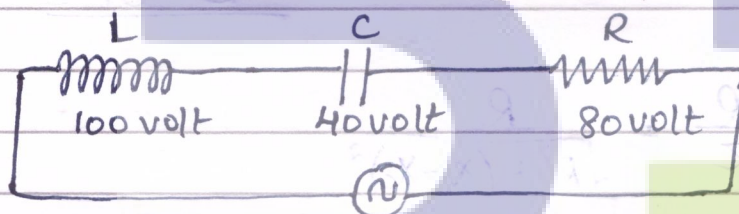

Find the Power factor?

Solu

$$V_R = 80 \text{ volt}, V_L = 100 \text{ volt}, V_C = 40 \text{ volt}$$

$$V_Z = \sqrt{V_R^2 + (V_L - V_C)^2} = \sqrt{(80)^2 + (100 - 40)^2}$$

$$\cos \phi = \frac{V_R}{V_Z} = \frac{80}{\sqrt{(80)^2 + (60)^2}} \Rightarrow \frac{80}{100} = \frac{4}{5}$$

Ques

In RL circuit Potential difference across Inductor (L) is 120 volt & potential difference across Resistance (R) is 90 volt. If rms value of current is 3A. What is Impedence of circuit & what is phase angle b/w voltage & Current?

Solu

$$V_L = 120 \text{ volt}, V_R = 90 \text{ volt}$$

$$I = 3A$$

As we know,

$$V = \sqrt{V_R^2 + (V_L - V_C)^2}$$



In RL circuit,  $V_C = 0$

$$V = \sqrt{V_R^2 + V_C^2}$$

$$V = \sqrt{(120)^2 + (90)^2} = \underline{150 \text{ volt}}$$

and  $V = IZ$

$$Z = \frac{V}{I} = \frac{150}{4} \Rightarrow \underline{37.5 \text{ ohm}}$$

$$\underline{Z = 37.5}$$

$$(ii) \tan \phi = \frac{R}{Z} = \frac{R}{\sqrt{R^2 + (X_L - X_C)^2}}$$

$$\tan \phi = \frac{V_R}{V}$$

#


### Resonance

- It is phenomenon of Resonance is common among a system that have tendency to oscillate at particular frequency called "Natural frequency of oscillation of system."
- If such a system in which a frequency is equal to natural frequency, the amplitude of oscillating become large called Resonance.

at Resonance,
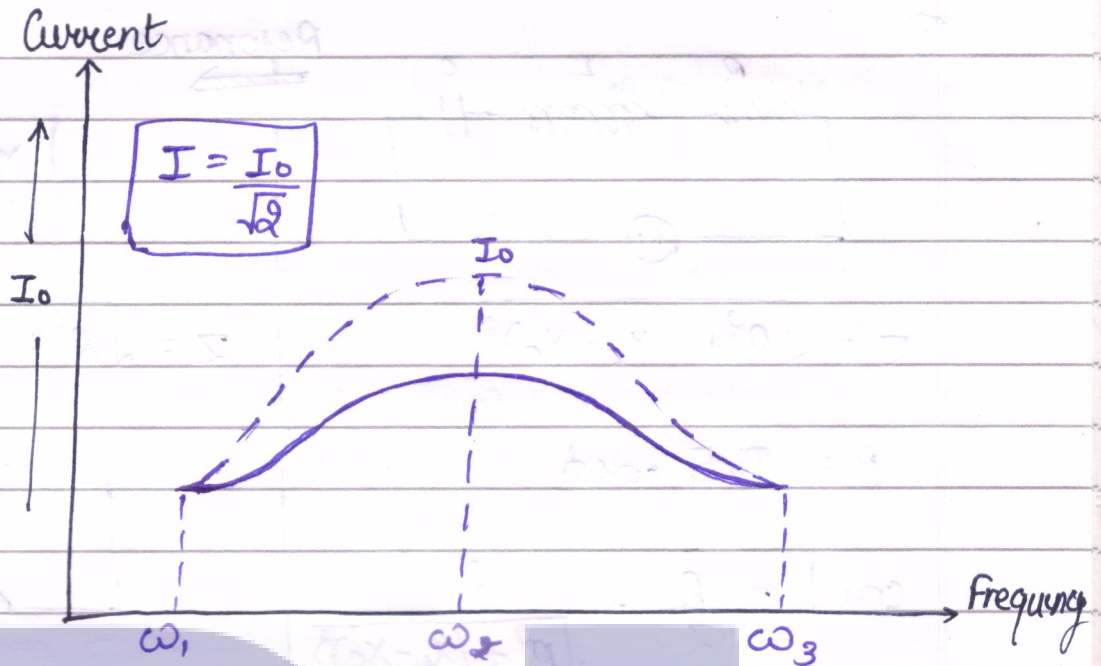
$$\underline{\text{Applied Frequency} = \text{Natural frequency}}$$





at Resonance

$$X_L = X_C$$

$$\omega L = \frac{1}{\omega C}$$

$$\omega^2 = \frac{1}{LC}$$

$$(2\pi\nu)^2 = \frac{1}{LC}$$

$$\nu^2 = \frac{1}{4\pi^2 LC}$$

$$\nu = \frac{1}{\sqrt{4\pi^2 LC}}$$

$$\nu = \frac{1}{2\pi\sqrt{LC}}$$

Resonance frequency

Note

1)  $X_L = X_C$


$X_L = \omega L$

$X_C = \frac{1}{\omega C}$

, Resonance frequency is

$$\nu = \frac{1}{2\pi\sqrt{LC}}$$

①

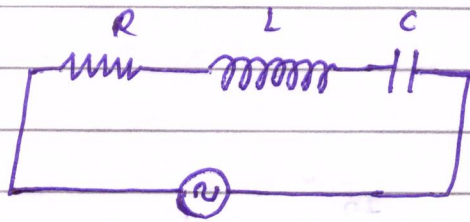

AT  
Resonance  
→


$$X_L = X_C$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$Z = \sqrt{R^2 + 0^2}, \quad \underline{Z = R}$$

$$P = I_V E_V \cos \phi$$
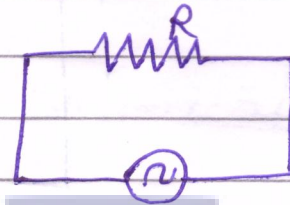
$$\cos \phi = \frac{R}{Z} = \frac{R}{\sqrt{R^2 + (X_L - X_C)^2}}$$



$$\rightarrow \cos \phi = 1$$

$$\tan \phi = \frac{X_L - X_C}{R} = \frac{V_L - V_C}{V_R}$$

$$\boxed{\phi = 0}$$

$$\rightarrow P = E_V I_V$$

$$X_L = \omega L = 2\pi \nu L$$

$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi \nu C}$$

$$\boxed{P = \frac{E_0}{\sqrt{2}} \times \frac{I_0}{\sqrt{2}} = \frac{E_0 I_0}{2}}$$

$$V = \sqrt{V_R^2 + (V_L - V_C)^2}$$

$$\boxed{V = V_R}$$

### Quality factor [sharpness of resonance]

→ It is ratio of voltage across Inductor or capacitor to applied voltage across R.

$$Q.F = \frac{V_L \text{ or } V_C}{V_R}$$

$$Q.F = \frac{V_L}{V_R}$$

$$Q.F = \frac{V_C}{V_R}$$



$$Q.F = \frac{V_L}{V_R}$$

$$Q.F = \frac{IX_L}{IR} = \frac{\omega L}{R}$$

$$Q.F = \frac{1}{\sqrt{LC}} \times \frac{L}{R} \Rightarrow \frac{1}{R} \sqrt{\frac{L}{C}}$$


$$Q.F = \frac{1}{R} \sqrt{\frac{L}{C}}$$

$$Q.F = \frac{V_C}{V_R}$$

$$Q.F = \frac{IX_C}{IR} = \frac{1}{\omega C} \times \frac{1}{R}$$

$$Q.F = \frac{1}{\frac{1}{\sqrt{LC}} \times C \times R} = \frac{1}{R} \sqrt{\frac{L}{C}}$$

graph

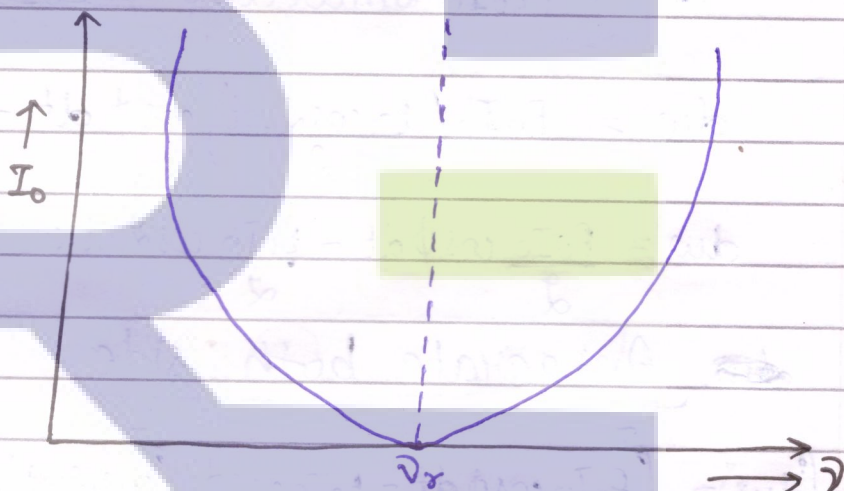

$\omega_r$  = Resonant frequency,

$$\omega_r = \frac{1}{2\pi\sqrt{LC}}$$

Average Power in LCR circuit (Inductive circuit)

Let, Applied emf to LCR circuit is  $E$  &  $E = E_0 \sin(\omega t)$   
& current is lag behind the applied emf by phase angle ( $\phi$ )

$$E = E_0 \sin(\omega t)$$

$$I = I_0 \sin(\omega t - \phi)$$



$$P = \frac{dw}{dt} = EI$$

→  $dw$  = small work done

$$dw = EI dt$$

$$dw = (E_0 \sin \omega t)(I_0 \sin(\omega t - \phi)) dt$$

$$dw = E_0 I_0 (\sin \omega t)(\sin(\omega t - \phi)) dt$$

$$dw = E_0 I_0 (\sin \omega t)(\sin \omega t \cos \phi - \cos \omega t \sin \phi) dt$$

$$dw = (E_0 I_0 \sin^2 \omega t \cos \phi - E_0 I_0 \sin \omega t \cos \omega t \sin \phi) dt$$

$$dw = E_0 I_0 \left( \frac{1 - \cos 2\omega t}{2} \right) \cos \phi dt - E_0 I_0 \left( \frac{2 \sin \omega t \cos \omega t}{2} \right) \sin \phi dt$$

$$dw = \frac{E_0 I_0 \cos \phi}{2} dt - \frac{E_0 I_0 \cos 2\omega t \cos \phi}{2} dt - E_0 I_0 \left( \frac{\sin 2\omega t}{2} \right) \sin \phi dt$$

Integrate both side

$$\int dw = \int_0^T \frac{E_0 I_0 \cos \phi}{2} dt - \frac{E_0 I_0 \cos \phi}{2} \int_0^T \cos(2\omega t) dt - \frac{E_0 I_0 \sin \phi}{2} \int_0^T \sin 2\omega t dt$$

$$w = \frac{E_0 I_0 \cos \phi}{2} [T]_0^T - \frac{E_0 I_0 \cos \phi}{2} \left[ \frac{\sin 2\omega t}{2\omega} \right]_0^T - \frac{E_0 I_0 \sin \phi}{2} \left[ -\frac{\cos 2\omega t}{2\omega} \right]_0^T$$

$$w = \frac{E_0 I_0 \cos \phi}{2} [T - 0] - \frac{E_0 I_0 \cos \phi}{2 \times 2\omega} [\sin 2\omega T - \sin 2\omega(0)] - \frac{E_0 I_0 \sin \phi}{2 \times 2\omega} [-\cos 2\omega T + \cos 2\omega(0)]$$

$$w = \frac{E_0 I_0}{2} \left[ \cos \phi \cdot T - \frac{\cos \phi}{2\omega} [\sin 4\pi] + \frac{\sin \phi}{2\omega} [\cos 4\pi] \right]$$

$$w = \frac{E_0 I_0}{2} \left[ T \cos \phi - \frac{\cos \phi}{2\omega} (0) + \frac{\sin \phi}{2\omega} [1 - 1] \right]$$



$$\rightarrow W = \frac{E_0 I_0 T \cos \phi}{2}$$

Here  $P = \frac{W}{T} \Rightarrow \frac{E_0 I_0 \times T \cos \phi}{2 \times T}$

$$P = \frac{E_0}{\sqrt{2}} \times \frac{I_0}{\sqrt{2}} \cos \phi \Rightarrow P = E_r I_r \cos \phi$$

In,  $P = E_r I_r \cos \phi$

If,  $\phi = 0 \rightarrow (R) \quad P = E_r I_r$

$\phi = -90^\circ \rightarrow (L) \quad P = 0$

$\phi = +90^\circ \rightarrow (C) \quad P = 0$

Ques

The instantaneous emf of A.C source is  $\varepsilon = E = 300 \sin 314 t$ . What is rms value of emf?

Ans

$$E = 300 \sin 314 t$$

Comparing with, eq<sup>n</sup>  $E = E_0 \sin \omega t$

then,  $E_0 = 300$

$$\omega = 314$$

As we know,

$$\omega = 2\pi \nu$$

$$314 = 2\pi \nu$$

$$\nu = \frac{314}{2\pi}$$

and,  $E = \frac{E_0}{\sqrt{2}} \Rightarrow \frac{300}{\sqrt{2}} \times \frac{\sqrt{2}}{\sqrt{2}}$

$$E_{rms} = 150\sqrt{2}$$



Ques In Instantaneous current of AC,  $I = 5 \sin(3/4)t$ .  
What is rms value of current?


Ans  $I = 5 \sin(3/4)t$   
comparing by eq<sup>n</sup>,  $I = I_0 \sin \omega t$   
we get,

$$\underline{I_0 = 5}, \quad \underline{\omega = 3/4}$$

As we know,

$$I_{rms} = \frac{I_0}{\sqrt{2}} \Rightarrow \underline{\underline{\frac{5}{\sqrt{2}} \text{ Ampere}}}$$

Ques Calculate the Alternating Current;

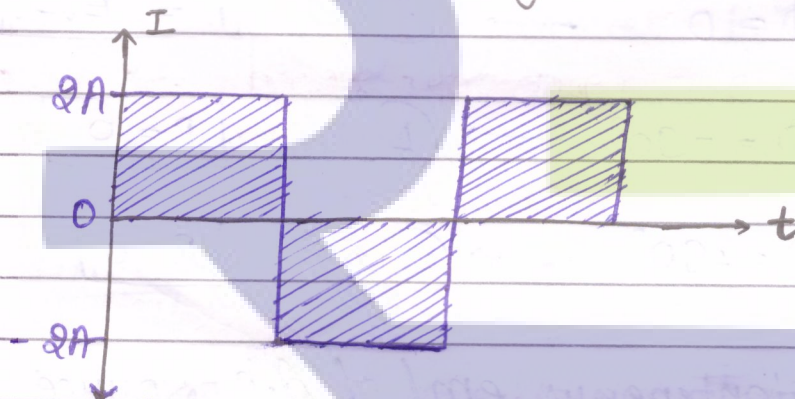

Ans 
$$I_{rms} = \sqrt{\frac{I_1^2 + I_2^2 + I_3^2}{3}} = \sqrt{\frac{(2)^2 + (-2)^2 + (2)^2}{3}} = \sqrt{\frac{4+4+4}{3}}$$
  
$$= \sqrt{\frac{12}{3}} = \sqrt{4} = \underline{\underline{2 \text{ Ampere}}}$$

Ques A pure Inductor of 25mH is connected to a, source of 220 volt, find the Inductive reactance and rms current in circuit if frequency of source is 50Hz?

Ans  $L = 25\text{mH} \Rightarrow 25 \times 10^{-3} \text{ H}$   
 $E_{rms} = 220 \text{ volt}, \quad f = 50\text{Hz}$





$$(i) \rightarrow X_L = \omega L$$

$$\rightarrow X_L = (2\pi f) L$$

$$= \frac{2 \times 22}{7} \times 50 \times 5 \times 10^{-3} \Rightarrow \frac{2 \times 22}{7} \times \frac{50 \times 25}{1000} = \frac{55}{7}$$

$$= \frac{55}{7} \Rightarrow \underline{\underline{7.8571}}$$

$$(ii) E_{rms} = I_{rms} (X_L)$$

$$\frac{E_{rms}}{X_L} = I_{rms}$$

$$\left[ \frac{220}{X_L} = I_{rms} \right] \Rightarrow \frac{220}{55} \times 7 \Rightarrow \underline{\underline{28.7272}}$$

Ques

Find the maximum value of current when : an Inductance of one henry is connected to an A.C source of 200 volt, 50 Hz.

Ans

$$f = 50 \text{ Hz}, E = 200 \text{ volt}, L = 1 \text{ H}$$

$$E_{rms} = I X_L$$

$$I = \frac{E_{rms}}{X_L} = \frac{200}{\omega L} \Rightarrow \frac{200}{2\pi f L}$$

$$= \frac{200 \times 7}{2 \times 22 \times 50} = \underline{\underline{0.6363}}$$

$$I_0 = I \times \sqrt{2} \Rightarrow \frac{7\sqrt{2}}{11} \Rightarrow \boxed{\frac{7\sqrt{2}}{11} \text{ A}}$$

$$I_0 = \frac{7}{11} \times 1.41 \Rightarrow \frac{9.87}{11} \Rightarrow \boxed{0.8972 \text{ A}}$$



Ques A coil has an Inductance of  $1\text{H}$

- (i) At what frequency will it have a reactance of  $3124\Omega$   
(ii) What should be capacity of a capacitor which has the same reactance at that frequency?

Ans (i)  $L = 1\text{H}$

$$X_L = \omega L = 2\pi f L$$

$$3124 = 2\pi f (1)$$

$$f = \frac{3124 \times 7}{2 \times 22} = \frac{21868}{44} \Rightarrow \underline{497\text{ Hz}}$$

(ii)  $X_L = X_C$  (same reactance),  $C = ?$

$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi f C}$$

$$C = \frac{1}{2\pi f \times X_C} \Rightarrow \frac{7}{2 \times 22 \times 497 \times 3124} = \frac{7}{68315632}$$

$$\Rightarrow \frac{7}{6.9 \times 10^7} \Rightarrow \underline{1.01 \times 10^{-7}\text{ F}}$$

Ques A  $1.50\mu\text{F}$  capacitor is connected to a  $22\text{volt}$ ,  $50\text{Hz}$  source, find the capacitive reactance & current (rms & peak) in circuit. If the frequency is doubled what happens to capacitive reactance and current?

Ans Given,  $C = 1.50\mu\text{F}$ ,  $E = 22\text{volt}$ ,  $f = 50\text{Hz}$

$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi f C}$$

$$X_C = \frac{7}{2 \times 22 \times 50 \times 1.50} \Rightarrow \frac{7}{3300} = \underline{0.00212}$$



As we know,  $E = I X_c$

$$\omega L = I \times X_c$$

$$I_{rms} = \frac{\omega L}{X_c} \Rightarrow \frac{\omega L \times 3300 \times 7}{3300}$$

$$= \frac{10241.4286}{3300} \Rightarrow \underline{\underline{0.0466 \text{ A}}}$$

$$I_o = I_{rms} \times \sqrt{2}$$

$$= 0.466 \times \sqrt{2}$$

$$= \underline{\underline{0.6505}}$$

If frequency is doubled then,  $\omega' = 2\omega$

$$X_c' = \frac{1}{2\pi \omega' C} \Rightarrow \frac{1}{2\pi (2\omega) C}$$

$$\boxed{X_c' = \frac{1}{2} X_c}$$

Inductor value is halved.

Inductor value is halved.

Inductor value is halved.

$$\left[ \begin{array}{l} \omega = 2\pi \times 50 \\ \omega' = 2\pi \times 100 \end{array} \right]$$

Inductor value is halved.

$$\left[ \begin{array}{l} \omega = 2\pi \times 50 \\ \omega' = 2\pi \times 100 \end{array} \right]$$


Inductor value is halved.



**RAHEIN EDUCATION**  
www.raheineducation.com

**PHYSICS**

## CBSE RESULT 2020

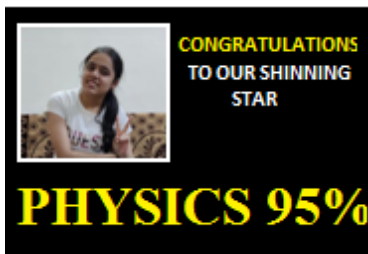

**Special Physics for NEET/JEE**

**Timing: 8:30a.m. to 10:30a.m. [Monday to Friday]**

**Saturday: Test**

**Fees: Rs. 25,000 and Online Test Series Rs. 1,000**

**Place: Rahein Education Pvt. Ltd.**

**Contact us: 9205010851, 9711833446**

**For Free Download Notes: [www.raheineducation.com](http://www.raheineducation.com)**

**E-mail: [tarunkumar.csengg@gmail.com](mailto:tarunkumar.csengg@gmail.com)**